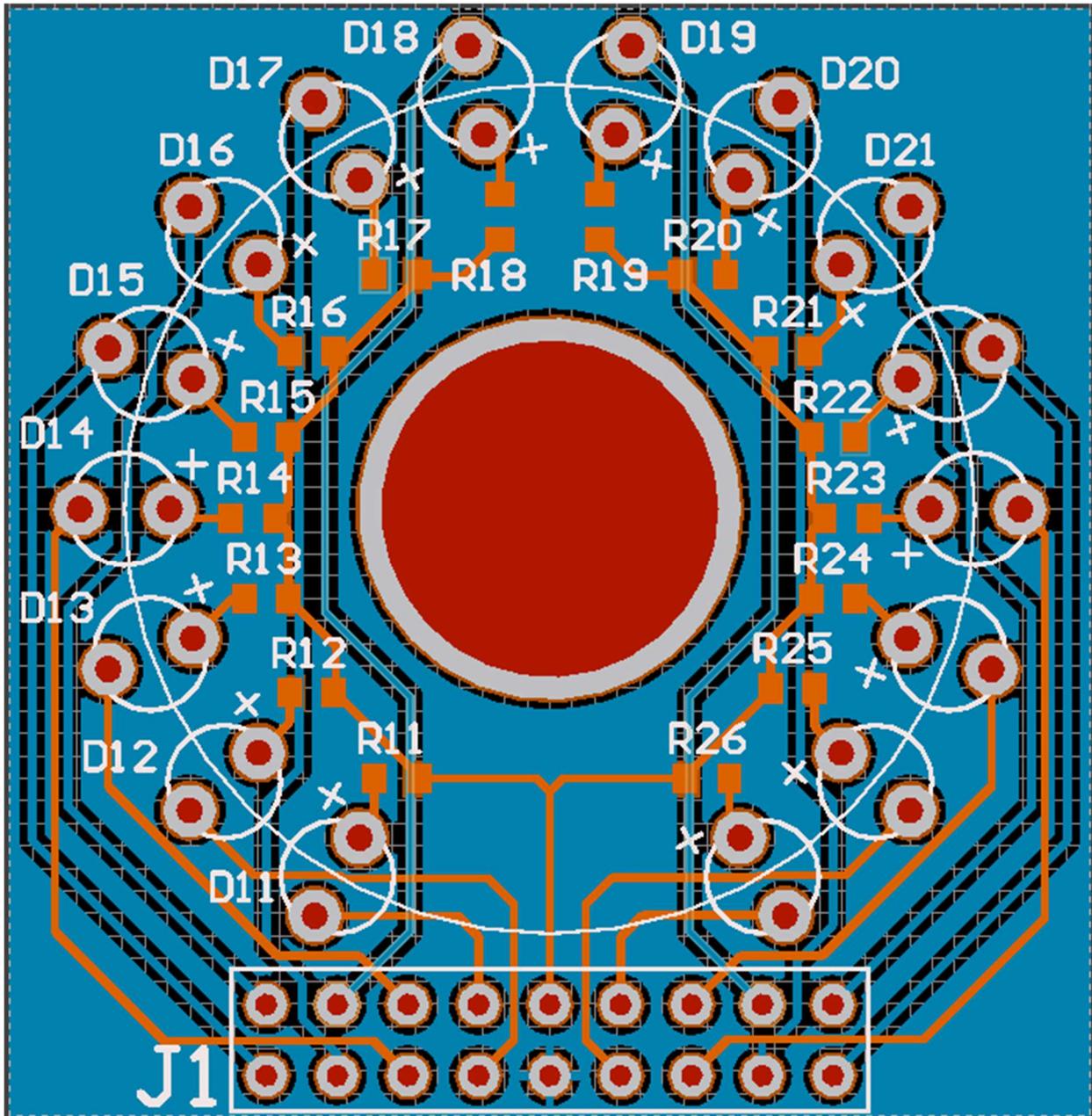


The first board for the LEDs is 1.230" x 1.2". I imagine with your experience you could find room to get the 30 mil back if it's an issue, but I try to keep my clearances reasonable because I have only had a half dozen or so boards actually made. I initially designed for a 1.6k 1% 0603 current limiting resistor but the 1.69k 1% 0603 house part from Macrofab should do fine. I also put in a ground plane just because it's for an audio device, but as far as the LEDs are concerned I don't think it does very much. Here's the board I designed.



I'm nowhere near as far on the second driver board. Basically, an oscillator drives a counter that controls which output is active on a demuxer that drives a buffer for the LEDs. The input value



AB26T-32.768KHZ Crystal - \$0.1588 each  
DM74ALS163BM Counter - \$0.0399 each @ 10+ qty  
CD4514BM96 Demux - \$0.5785 each @ 10+ qty  
CD14538BPW Multivibrator - \$0.3952 each @ 10+ qty  
MC74LCX16244DTG Buffer - \$0.3968 each

Total \$1.7422 in IC's per unit + ~25 jelly bean components like standard value 1% resistors and standard value caps. As far as LEDs go I designed for the TLLG4400 from Vishay which is \$0.1324 each @ 250 qty, but I imagine there are more economic ways to find 400 standard green T-1 LEDs. The current limiting diode is pretty conservative so you could even use yellow and red LED's to indicate that a pot is turned all the way up.

Brett Smith